

Mechanical Systems & RLC Circuits

Dynamical Systems

Major sources:

Major references:

Winter 2022 - Dan Calderone

RLC Circuits

FIRST ORDER SYSTEMS

(1st order derivatives)

Diagrams

Dynamics

Mechanical Analogs


RC Circuits

Capacitor state:


charge or voltage

(proportional)

$$V_C = CQ_C$$

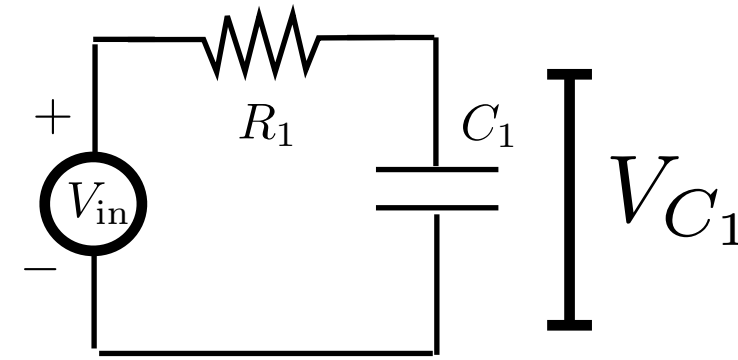
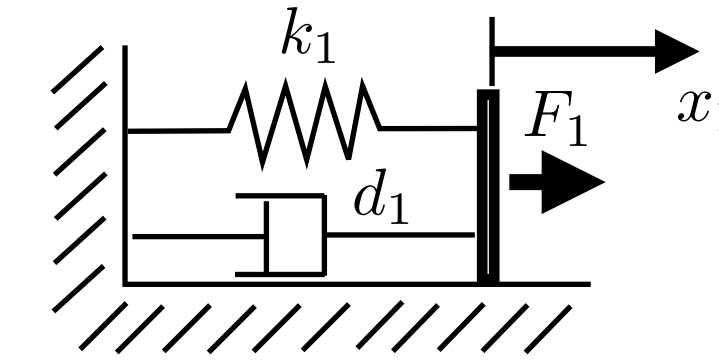
$$\dot{Q} = -\frac{C}{R}Q + \frac{1}{R}V_{in}$$




Compression spring
(no mass, stores energy)

RL Circuits


Inductor state:

current

$$I_L$$

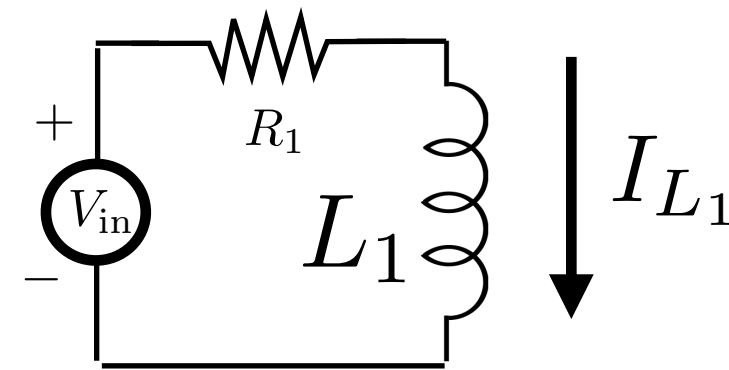
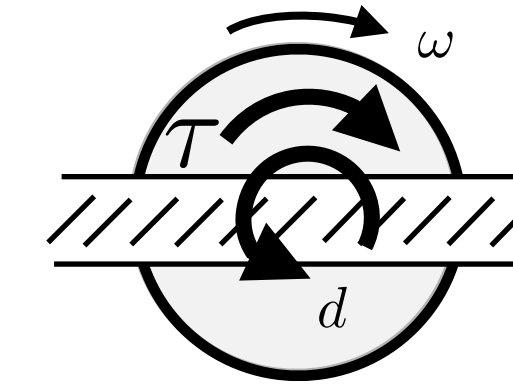
$$\dot{I} = -\frac{R}{L}I + \frac{1}{L}V_{in}$$



Flywheel with angular momentum
(no position, only angular velocity)

SECOND ORDER SYSTEMS

(2nd order derivatives)

RLC Circuits

... one state per object with dynamics

States:



Capacitor state: charge or voltage

(proportional)

...analogous to position

Inductor state: current

...analogous to velocity

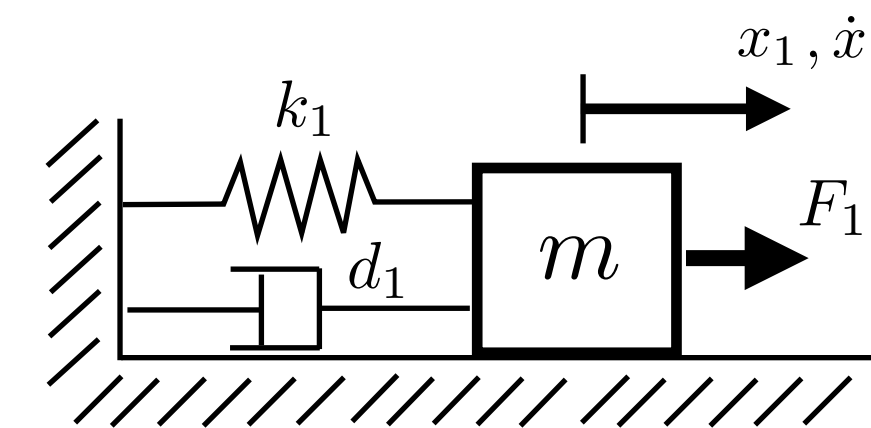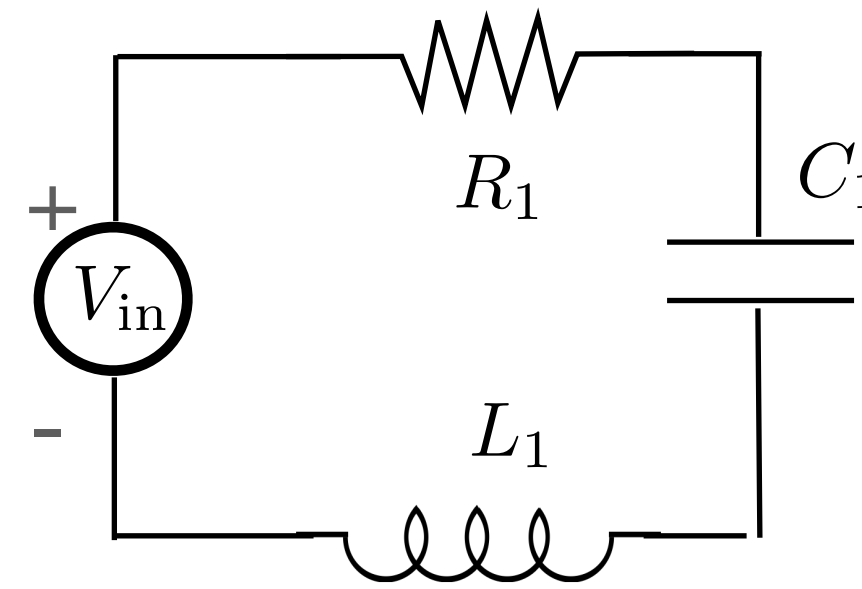

Dynamics:

Graph Relations:

Elements:

$$\dot{Q}_C = I_C$$

KVL: sum of voltage around a loop = 0

$$V_C = CQ_C$$

$$L\dot{I}_L = V_L$$

KCL sum of currents into a node = 0

$$V_R = RI_R$$

$$V_L = L\dot{I}_L$$

RLC Circuits

FIRST ORDER SYSTEMS

(1st order derivatives)

Diagrams

Dynamics

Mechanical Analogs


RC Circuits

Capacitor state:


charge or voltage

(proportional)

$$V_C = CQ_C$$

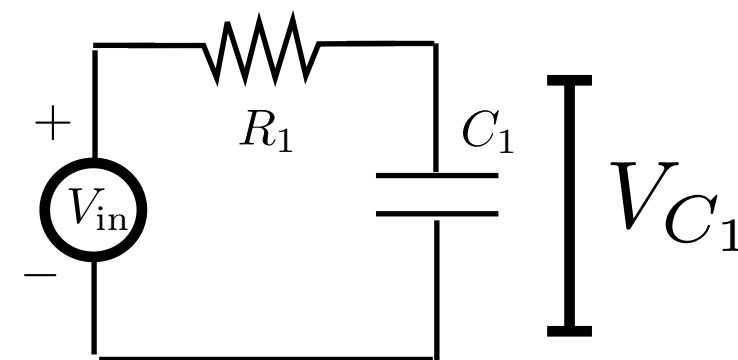
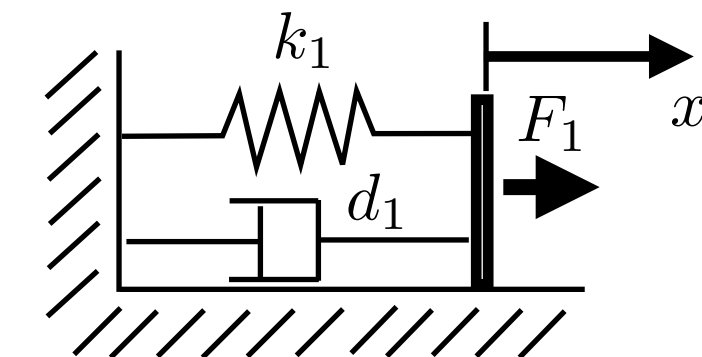
$$\dot{Q} = -\frac{C}{R}Q + \frac{1}{R}V_{in}$$




Compression spring
(no mass, stores energy)

RL Circuits


Inductor state:

current

$$I_L$$

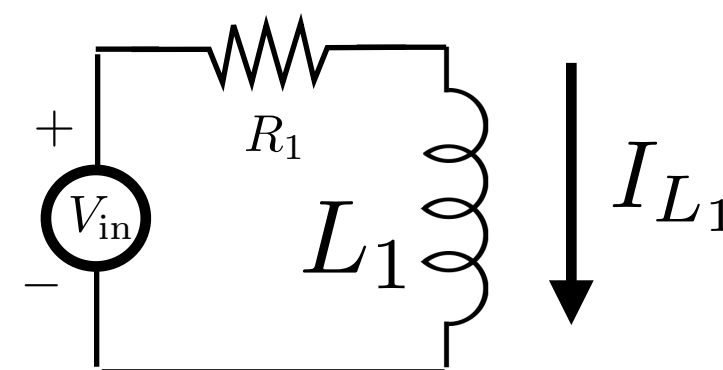
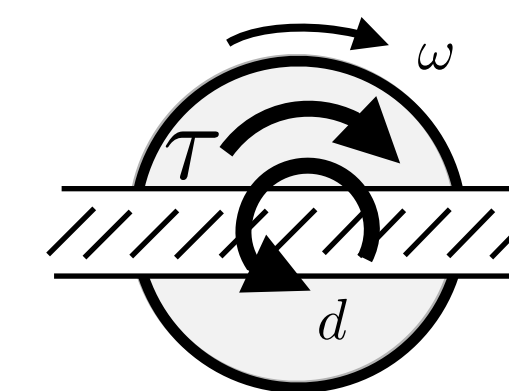
$$\dot{I} = -\frac{R}{L}I + \frac{1}{L}V_{in}$$



Flywheel with angular momentum
(no position, only angular velocity)

SECOND ORDER SYSTEMS

(2nd order derivatives)

RLC Circuits

... one state per object with dynamics

States:

Capacitor state: charge or voltage

(proportional)

Inductor state: current

...analogous to position

...analogous to velocity

Dynamics:

$$\dot{Q}_C = I_C$$

$$L\dot{I}_L = V_L$$

Graph Relations:

KVL: sum of voltage around a loop = 0


KCL: sum of currents into a node = 0

Elements:

$$V_C = CQ_C$$

$$V_R = RI_R$$

$$V_L = LI_L$$

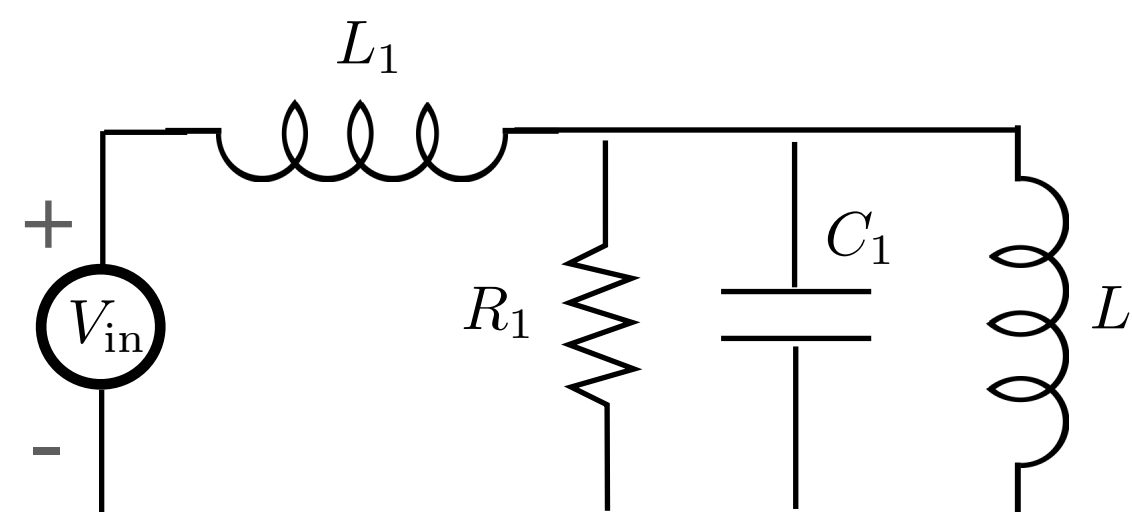

States:

Q_{C_1} Charge on capacitor 1

I_{L_1} Current thru inductor 1

I_{L_2} Current thru inductor 2

KVL/KCL Equations:

$$\text{KVL: } V_{in} = V_{L_1} + V_{R_1}$$

$$V_{R_1} = V_{C_1} = V_{L_2}$$

$$\text{KCL: } I_{L_1} = I_{R_1} + I_{C_1} + I_{L_2}$$

Derived in terms of states...

$$V_{C_1} = V_{R_1} = V_{L_2} = C_1 Q_{C_1}$$

$$V_{L_1} = V_{in} - C_1 Q_{C_1}$$

$$I_{R_1} = \frac{C_1}{R_1} Q_{C_1}$$

$$I_{C_1} = I_{L_1} - I_{L_2} - \frac{C_1}{R_1} Q_{C_1}$$

Dynamics:

$$\dot{Q}_{C_1} = I_{C_1} = I_{L_1} - I_{L_2} - \frac{C_1}{R_1} Q_{C_1}$$

$$L_1 \dot{I}_{L_1} = V_{L_1} = V_{in} - C_1 Q_{C_1}$$

$$L_2 \dot{I}_{L_2} = V_{L_2} = C_1 Q_{C_1}$$